

**AIM:**

To simulate and synthesis ENCODER, DECODER, MULTIPLEXER, DEMULTIPLEXER, MAGNITUDE COMPARATOR using Xilinx ISE.

**APPARATUS REQUIRED:**

Xilinx 14.7 Spartan6 FPGA

**PROCEDURE:****STEP:1**

Start the Xilinx navigator, Select and Name the New project.

**STEP:2**

Select the device family, device, package and speed.

**STEP:3**

Select new source in the New Project and select Verilog Module as the Source type.

**STEP:4**

Type the File Name and Click Next and then finish button. Type the code and save it.

**STEP:5**

Select the Behavioral Simulation in the Source Window and click the check syntax.

**STEP:6**

Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

**STEP:7**

Select the Implementation in the Sources Window and select the required file in the Processes Window.

**STEP:8**

Select Check Syntax from the Synthesize XST Process. Double Click in the FloorplanArea/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.

**STEP:9**

In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.

**STEP:10**


Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.

### STEP:11


On the board, by giving required input, the LEDs starts to glow light, indicating the output.

### LOGIC DIAGRAM:


#### ENCODER:

 


DECODER:

 

## MULTIPLEXER:

 

## DEMULTIPLEXER:

 

## MAGNITUDE COMPARATOR:



## VERILOG CODE:

### ENCODER:

```
module encoder(i,o);  
  
input [7:0]i;  
  
output [2:0]o;  
  
or g1(o[0],i[1],i[3],i[5],i[7]);  
  
or g2(o[1],i[2],i[3],i[6],i[7]);  
  
or g3(o[2],i[4],i[5],i[6],i[7]);  
  
endmodule
```

### DECODER:

```
module decoder(a,y);  
  
input [2:0]a;  
  
output [7:0]y;  
  
wire w0,w1,w2;
```

```

not g1(w0,a[0]);

not g2(w1,a[1]);

not g3(w2,a[2]);

and g4(y[0],w0,w1,w2);

and g5(y[1],w2,w1,a[0]);

and g6(y[2],w2,a[1],w0);

and g7(y[3],w2,a[1],a[0]);

and g8(y[4],a[2],w1,w0);

and g9(y[5],a[2],w1,a[0]);

and g10(y[6],a[2],a[1],w0);

and g11(y[7],a[2],a[1],a[0]);

endmodule

```

## **MULTIPLEXER:**

```

module mux81(d,s,y);

input [7:0]d;

input [2:0]s;

output y;

wire w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11;

not g1(w1,s[0]);

not g2(w2,s[1]); not g3(w3,s[2]);

and g4(w4,d[0],w1,w2,w3);

and g5(w5,d[1],w1,w2,s[2]);

and g6(w6,d[2],w1,w3,s[1]);

and g7(w7,d[3],w1,s[1],s[2]);

```

```

and g8(w8,d[4],s[0],w2,w3);

and g9(w9,d[5],s[0],s[2],w2);

and g10(w10,d[6],s[0],s[1],w3);

and g11(w11,d[7],s[0],s[1],s[2]);

or g12(y,w4,w5,w6,w8,w9,w10,w11);

endmodule

```

## DE-MULTIPLEXER:

```

module demux8x1(d,s,y);

input d;

input [2:0]s;

output [7:0]y;

wire w1,w2,w3;

not g1(w1,s[0]);

not g2(w2,s[1]);

not g3(w3,s[2]);

and g4(y[0],d,w1,w2,w3);

and g5(y[1],d,w1,s[0],w3);

and g6(y[2],d,w3,s[1],w1);

and g7(y[3],d,s[0],s[1],w3);

and g8(y[4],d,s[2],w1,w2);

and g9(y[5],d,s[2],s[0],w2);

and g10(y[6],d,w1,s[1],s[2]);

and g11(y[7],d,s[2],s[1],s[0]);

```

```
endmodule
```

### **MAGNITUDE COMPARATOR:**

```
module magnitude(a,b,greater,lesser,equal);
```

```
input[2:0]a,b;
```

```
output reg greater,lesser,equal;
```

```
always @(*)
```

```
begin
```

```
if (a>b)
```

```
begin
```

```
greater=1'b1;
```

```
lesser=1'b0;
```

```
equal=1'b0;
```

```
end
```

```
else if(a<b)
```

```
begin
```

```
greater=1'b0;
```

```
lesser=1'b1;
```

```
equal=1'b0;
```

```
end
```

```
else
```

```
begin
```

```
greater=1'b0;
```

```
lesser=1'b0;
```

```
equal=1'b1;
```




end

end


endmodule

## OUTPUT WAVEFORM:


### ENCODER:

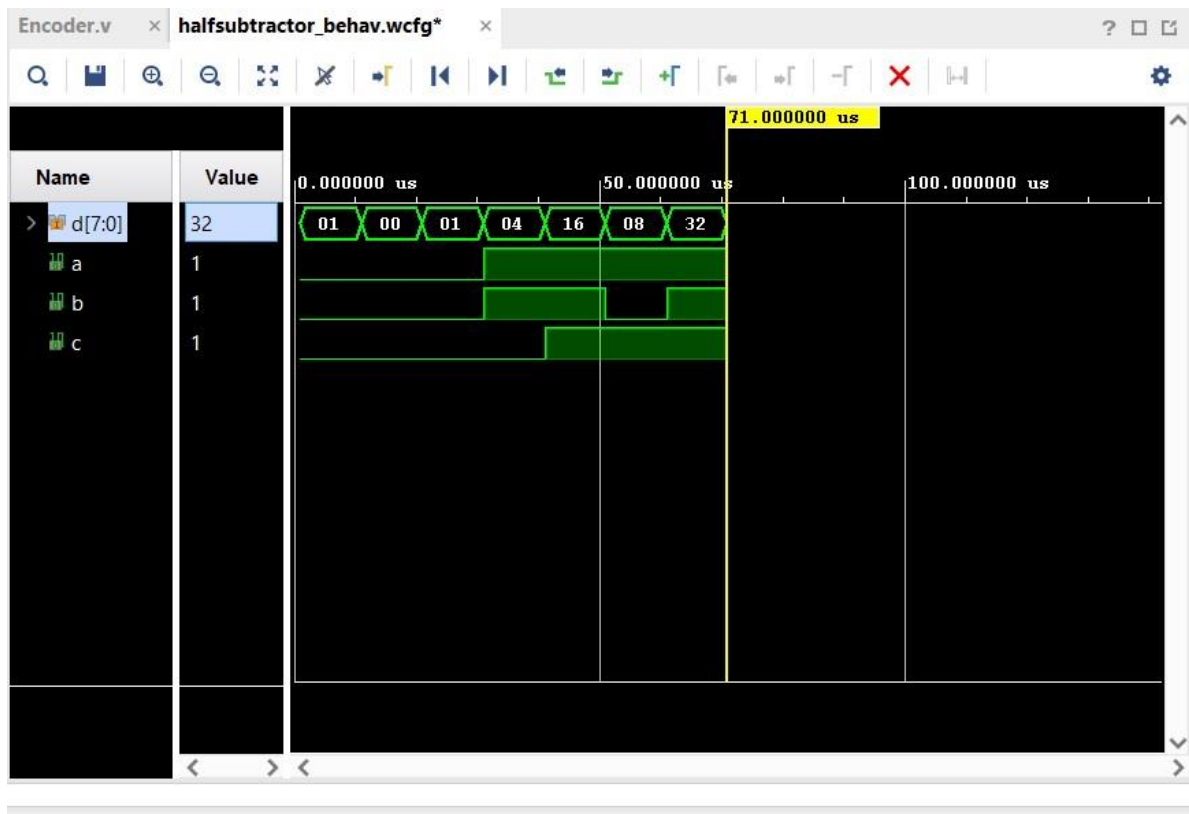

## DECODER:

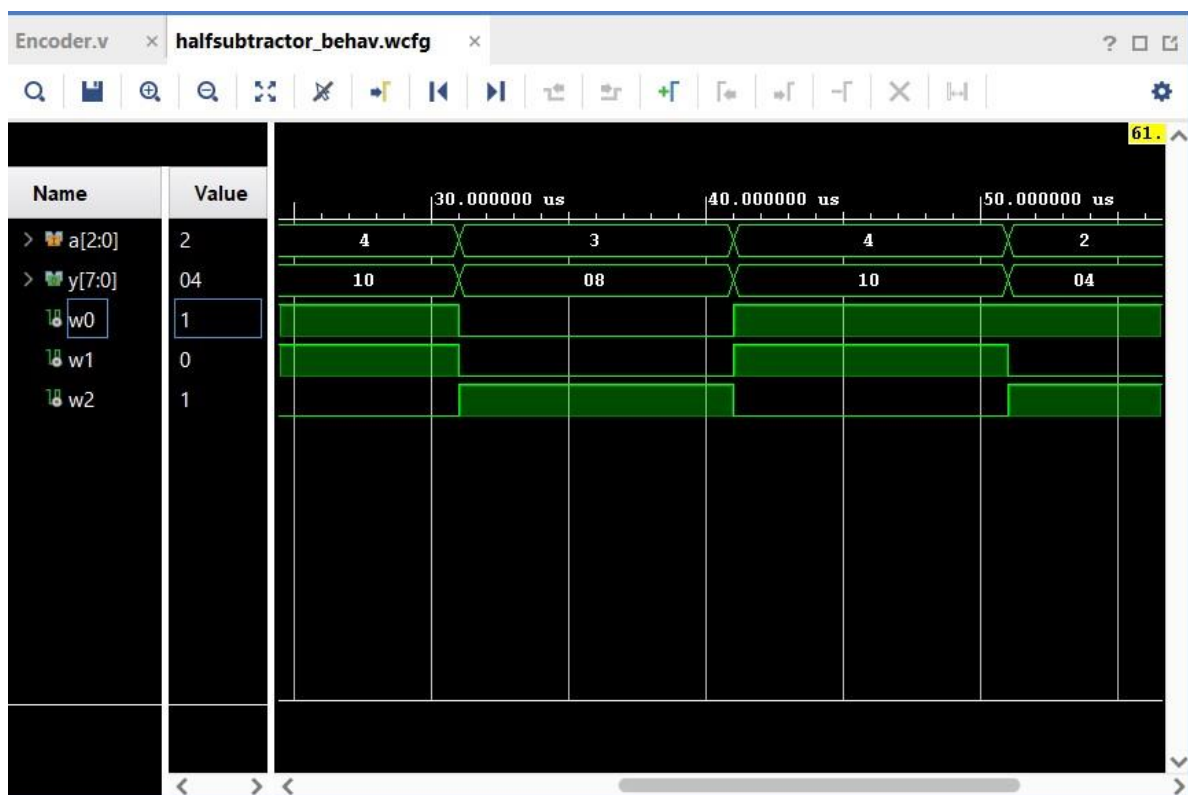


**MULTIPLEXER:**

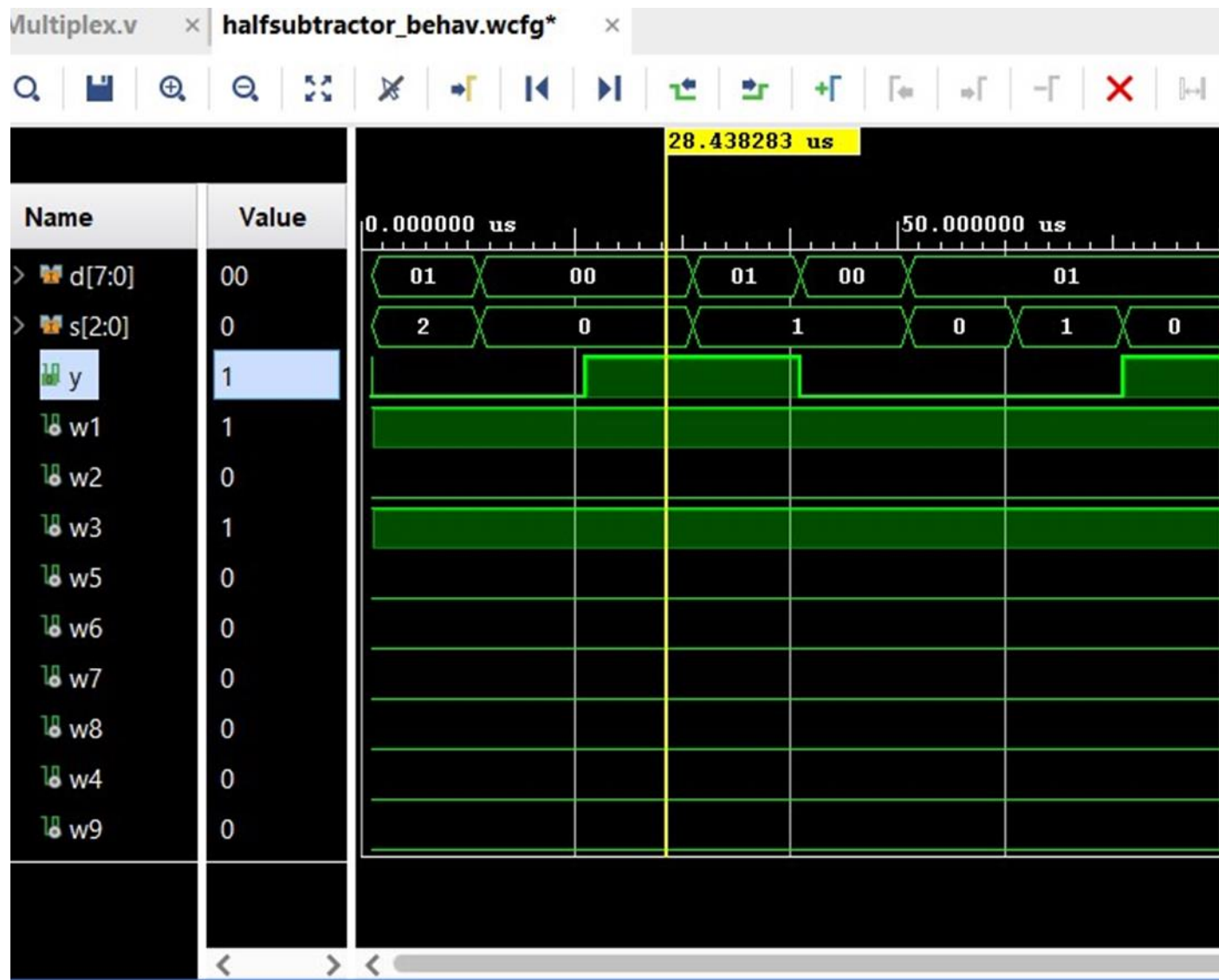

DE-MULTIPLEXER:



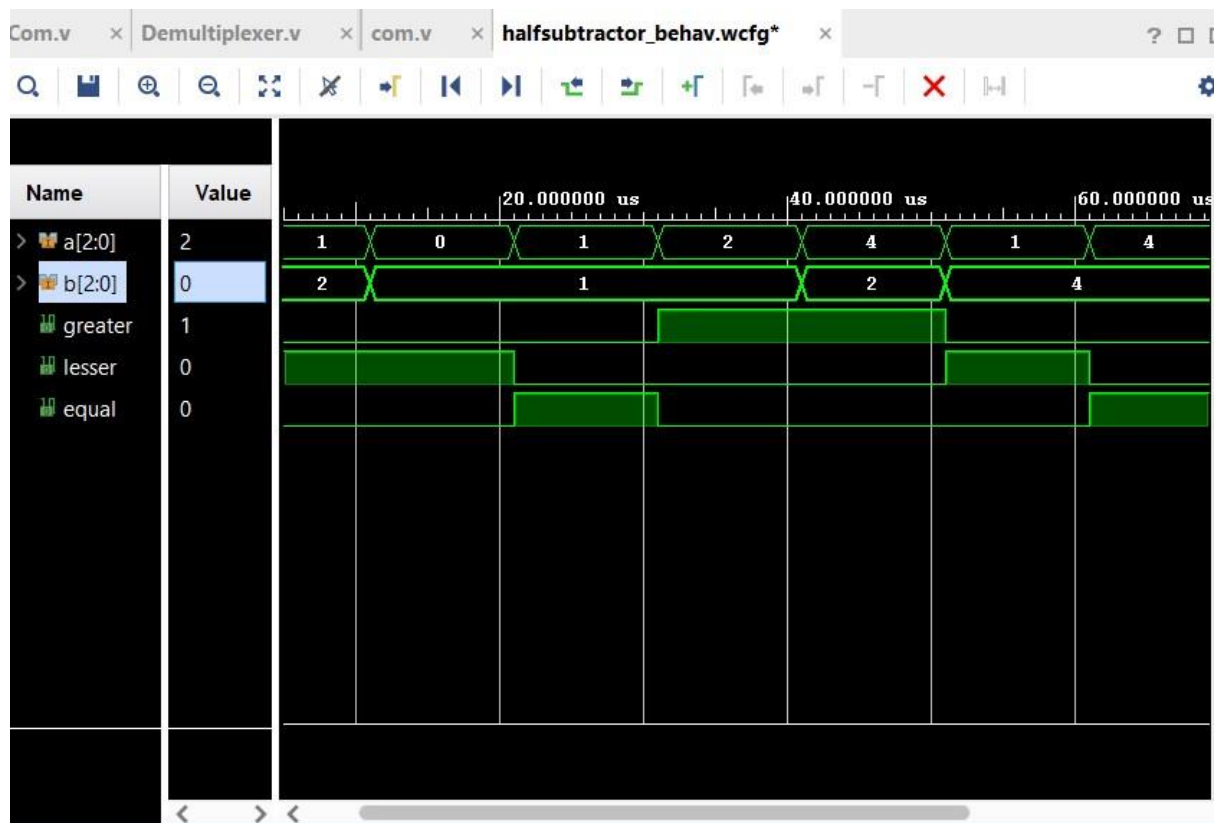

### RESULT:

Hence, The simulation and synthesis Encoder, Decoder, Multiplexer, Demultiplexer, Magnitude Comparator was running successfully using Xilinx ISE.